Time on		

Total time_

Time off_

CDX Tasksheet Number: C291

- Test for proper operation of the test light by connecting it across the vehicle's battery terminals.
 - a. Connect the clip end (negative) of the test light to the negative battery terminal.
 - b. Touch the probe end of the test light to the positive battery terminal. The test light should light.
 - c. Did the test light operate correctly? Yes: _____ No: ____

NOTE Please notify your supervisor/instructor if the test light did not operate correctly.


2. Using the wiring diagram for the left tail lamp/parking light circuit of the assigned vehicle, identify the wire color for both the power (voltage) and ground (negative) wire.

> i. Power (positive): ii. Ground (negative): __

- 3. Using the appropriate tools, remove the taillight assembly and disconnect the tail lamp connector. The headlamp switch should be set to "Off."
 - a. Visually locate the power and ground wires, as described in step 2.
 - b. Turn the headlamp switch to the "Park" position.
 - c. Connect the clip end of the test light to an unpainted metal surface that is a good ground.
 - d. Touch the test light probe to the positive wire of the vehicle harness tail lamp connector cavity.
 - i. Did the test light come on? Yes: _____ No: ____
 - ii. Please explain your results:
 - e. With the test light probe still connected to the positive wire, test the ground wire by removing the clip end of the test light and touching it to the ground wire of the tail lamp connector cavity, being careful not to cause a short circuit by touching the clip to the probe. The light should come on if there is a good ground.

i. Did the light come on? Yes: _____ No:

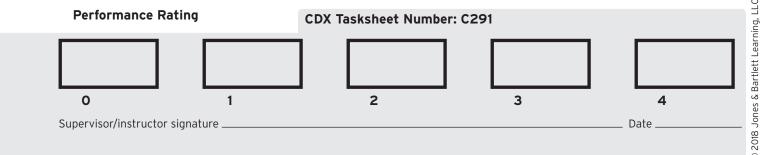3. Based on your observations, determine any necessary action(s):



816 Electrical/Electronic Systems