► TASK Use wiring diagrams during the diagnosis (troubleshooting) of electrical/electronic circuit problems.

Time off_	

Time on\_

CDX Tasksheet Number: C952

NOTE This task requires diagnosis of an electrical problem. Please ask your instructor/supervisor to assign you a vehicle that qualifies for this task and several that follow.

Total time\_

- 1. List the customer concern/complaint:
- 2. Which electrical circuit(s) are involved?
- 3. How many circuit protection devices are there in this circuit?
  - a. List the circuit protection devices in this circuit:
  - b. List the circuit control devices in this circuit:
  - c. Which side of the load(s) is controlled?
- 4. Diagnose the fault and list each test and its result:

- 5. Determine any necessary actions:
- 6. Have your supervisor/instructor verify satisfactory completion of this procedure, any observations found, and any necessary action(s) recommended.

**Performance Rating** CDX Tasksheet Number: C952 0 2 3 4 Supervisor/instructor signature \_ Date\_

812 Electrical/Electronic Systems